

- 4.2 Trace the behavior of an 8-bit parallel-load register with 8-bit input I , 8-bit output Q , load control input ld , and synchronous clear input clr by completing the timing diagram in Figure 4.96.

 


Figure 4.96 Timing diagram.

- 4.3 Design a 4-bit register with 2 control inputs s_1 and s_0 ; 4 data inputs I_3, I_2, I_1 , and I_0 ; and 4 data outputs Q_3, Q_2, Q_1 , and Q_0 . When $s_1s_0=00$, the register maintains its value. When $s_1s_0=01$, the register loads $I_3...I_0$. When $s_1s_0=10$, the register clears itself to 0000. When $s_1s_0=11$, the register complements itself, so for example, 0000 would become 1111, and 1010 would become 0101. (Component design problem.)
- 4.10 Assuming AND gates have a delay of 2 ns, OR gates have a delay of 1 ns, and XOR gates have a delay of 3 ns, compute the longest time required to add two numbers using an 8-bit carry-ripple adder.
- 4.13 Design an adder that computes the sum of four 8-bit numbers, using 8-bit carry-ripple adders. (Component use problem.)
- 4.21 Use magnitude comparators and logic to design a circuit that computes the maximum of two 16-bit numbers. (Component use problem.)
- 4.30 Convert the following two's complement binary numbers to decimal numbers:
- 11100000
 - 01111111
 - 11110000
 - 11000000
 - 11100000
- 4.33 Convert the following decimal numbers to 8-bit two's complement binary form:
- 29
 - 100
 - 125
 - 29
 - 100
 - 125
 - 2

- 4.40 Design an ALU with two 8-bit inputs A and B , and control inputs x , y , and z . The ALU should support the operations described in Table 4.3. Use an 8-bit adder and an arithmetic/logic extender. (*Component design problem.*)

TABLE 4.3 Desired ALU operations.

Inputs			Operation
x	y	z	
0	0	0	$S = A - B$
0	0	1	$S = A + B$
0	1	0	$S = A * 8$
0	1	1	$S = A / 8$
1	0	0	$S = A \text{ NAND } B$ (bitwise NAND)
1	0	1	$S = A \text{ XOR } B$ (bitwise XOR)
1	1	0	$S = \text{Reverse } A$ (bit reversal)
1	1	1	$S = \text{NOT } A$ (bitwise complement)

- 4.62 Design a 4x4 three-port (2 read, 1 write) register file. (*Component design problem.*)

- 4.64 A 4x4 register file's four registers initially each contain 0101.

- Show the input values necessary to read register 3 and to simultaneously write register 3 with the value 1110.
- With these values, show the register file's register values and output values before the next rising clock edge, and after the next rising clock edge.