

# CSCE 312 Lab 2

Kevin Lei

February 11, 2024

## 1 Problem 1

### 1.1 Part 1

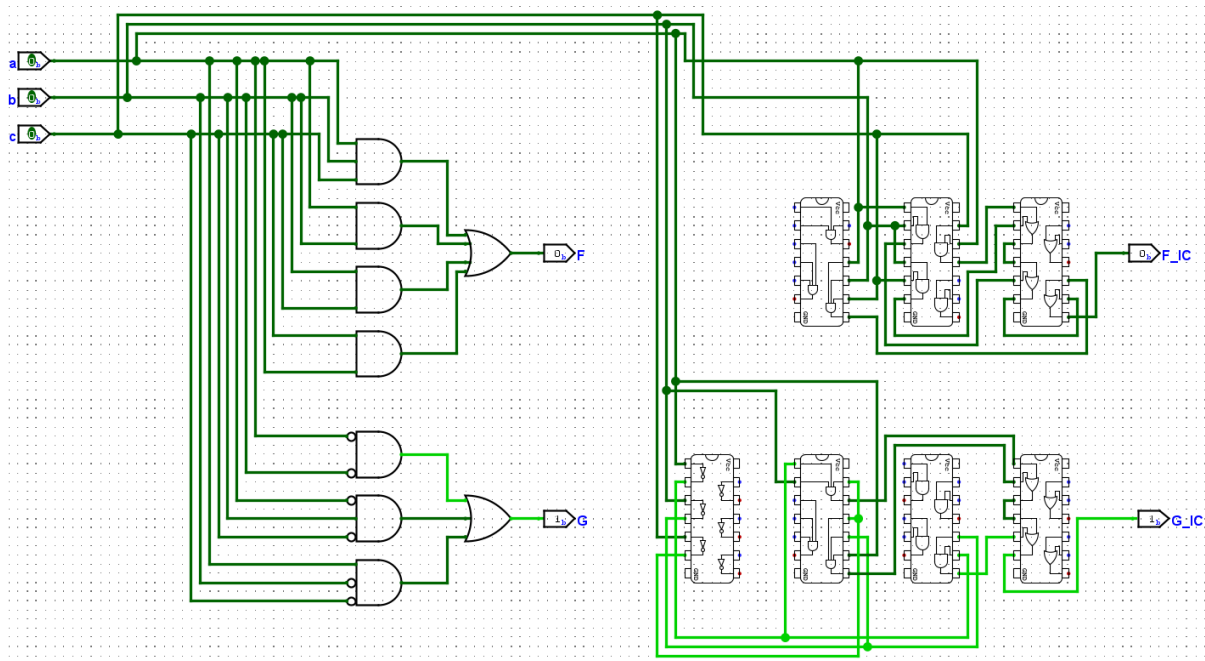


Figure 1: Implementations of boolean functions  $F$  and  $G$  using only logic gates and only 74xx series ICs.

ICs used in the implementation of boolean function  $F$ :

- 7408 quad 2-input AND gate
- 7411 triple 3-input AND gate
- 7432 quad 2-input OR gate

ICs used in the implementation of boolean function  $G$ :

- 7404 hex inverter
- 7408 quad 2-input AND gate
- 7411 triple 3-input AND gate
- 7432 quad 2-input OR gate

## 1.2 Part 2

For the pure logic gate implementations, we will assume a 22 nanosecond delay for each AND, OR, and NOT gate. The propagation delays for the 74xx series ICs are as follows:

- 7404: 22 ns
- 7408: 22 ns
- 7411: 22 ns
- 7432: 22 ns

Thus, the propagation delays for the implementations of  $F$  and  $G$  are as follows:

- $F$  (logic gates): 22 ns + 22 ns = 44 ns
- $G$  (logic gates): 22 ns + 22 ns + 22 ns = 66 ns
- $F$  (74xx series ICs): 22 ns + 22 ns = 44 ns
- $G$  (74xx series ICs): 22 ns + 22 ns + 22 ns = 66 ns

## 1.3 Part 3

Switching characteristics of 7404 hex inverter at  $V_{cc} = 5V$  and  $25^\circ C$ :

Symbol	Parameter	Conditions	Min	Typ	Max	Units
t <sub>plh</sub>	Propagation Delay Time LOW-to-HIGH Level Output	Cl=15pF Rl=400R			22	ns
t <sub>p<sub>hl</sub></sub>	Propagation Delay Time HIGH-to-LOW Level Output	Cl=15pF Rl=400R			15	ns

Switching characteristics of 7408 quad 2-input AND gate at  $V_{cc} = 5V$  and  $25^\circ C$ :

Symbol	Parameter	Conditions	Min	Typ	Max	Units
t <sub>plh</sub>	Propagation Delay Time LOW-to-HIGH Level Output	Cl=15pF Rl=400R			22	ns
t <sub>p<sub>hl</sub></sub>	Propagation Delay Time HIGH-to-LOW Level Output	Cl=15pF Rl=400R			15	ns

Switching characteristics of 7411 triple 3-input AND gate at  $V_{cc} = 5V$  and  $25^\circ C$ :

Symbol	Parameter	Conditions	Min	Typ	Max	Units
t <sub>plh</sub>	Propagation Delay Time LOW-to-HIGH Level Output	Cl=15pF Rl=400R			22	ns
t <sub>p<sub>hl</sub></sub>	Propagation Delay Time HIGH-to-LOW Level Output	Cl=15pF Rl=400R			15	ns

Switching characteristics of 7432 quad 2-input OR gate at  $V_{cc} = 5V$  and  $25^\circ C$ :

Symbol	Parameter	Conditions	Min	Typ	Max	Units
t <sub>plh</sub>	Propagation Delay Time LOW-to-HIGH Level Output	Cl=15pF Rl=400R			22	ns
t <sub>p<sub>hl</sub></sub>	Propagation Delay Time HIGH-to-LOW Level Output	Cl=15pF Rl=400R			15	ns

## 2 Problem 2

### 2.1 Part 1

- The number of input bits is 10 since there are 10 cars with switches.
- We will need 7 output bits for the 7-segment display (since each segment must be either on or off).
- We will need a 4-bit data bus between the encoder and decoder, since  $\lceil \log_2 10 \rceil = 4$ .
- We will need a 16:4 encoder. We will only need 10 of the 16 possible inputs.
- We will need a 4:16 decoder. We will only need 7 of the 16 possible outputs.

### 2.2 Part 2

The 7-segment display is simply just a combination of 7 LEDs arranged in a pattern to display the numbers 0-9. Each LED has its own input, and the display is controlled by turning on the appropriate LEDs to form the desired number. There is also a decimal point LED, but it is not used in this lab. Although the logical inputs to the display take up 8 pins, there are typically two more pins for the common anode or cathode, depending on the type of 7-segment display used.

### 2.3 Part 3

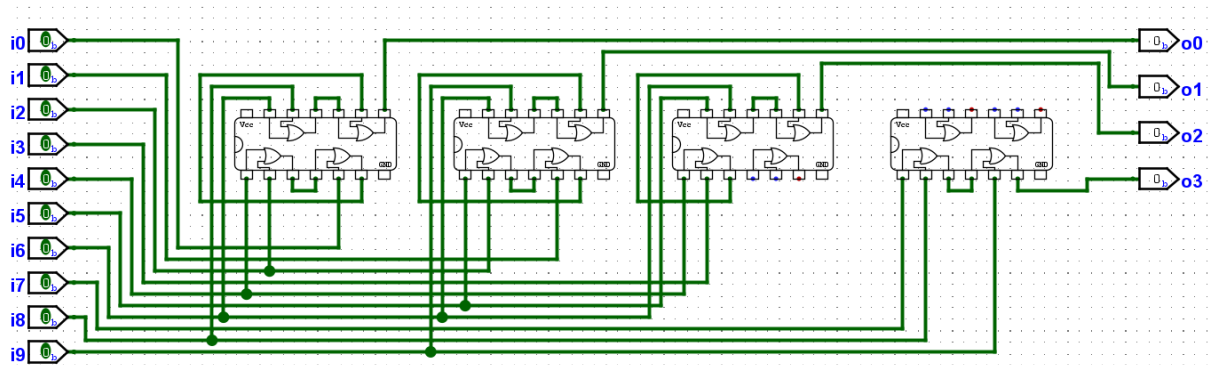


Figure 2: Encoder design

 


Figure 3: Decoder design

## 2.4 Part 4

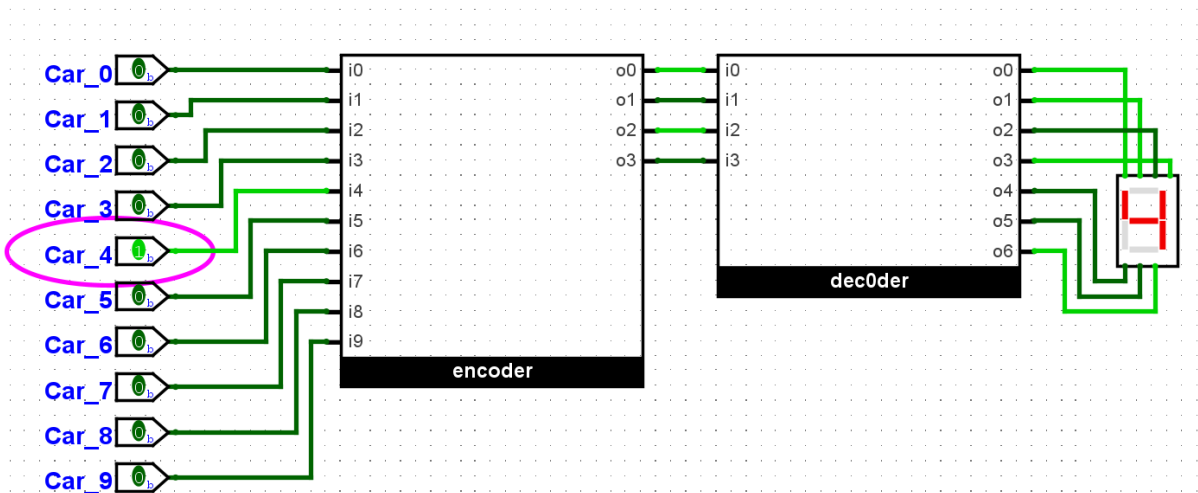


Figure 4: Overall circuit design

With the encoder and decoder abstracted away, the overall circuit design is relatively simple. The system works by having ten switches, each representing a car labeled from 0 to 9. It is assumed that no more than one switch will be on at a time. All ten switches are fed into the 16:4 encoder, which outputs a 4-bit binary number representing the car number. This 4-bit number is then fed into the 4:16 decoder, which outputs the 7-segment display signals for the corresponding number.