

# CSCE 312 Lab 2

Kevin Lei

February 11, 2024

## 1 Problem 1

### 1.1 Part 1

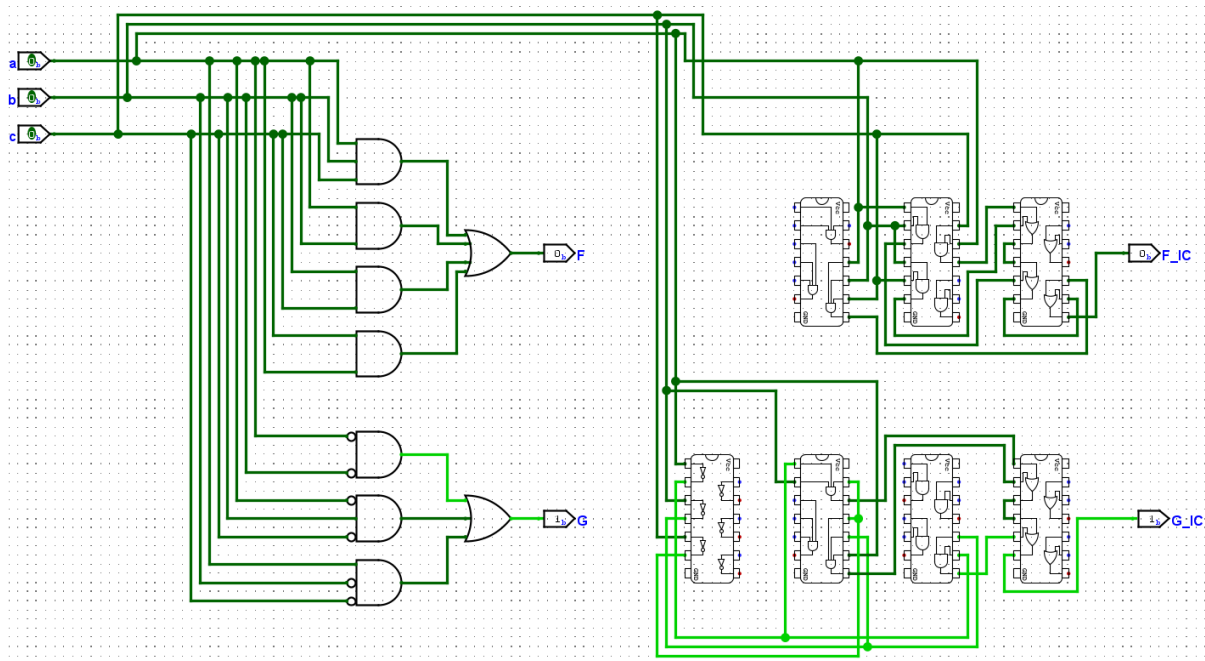


Figure 1: Implementations of boolean functions  $F$  and  $G$  using only logic gates and only 74xx series ICs.

ICs used in the implementation of boolean function  $F$ :

- 7408 quad 2-input AND gate
- 7411 triple 3-input AND gate
- 7432 quad 2-input OR gate

ICs used in the implementation of boolean function  $G$ :

- 7404 hex inverter
- 7408 quad 2-input AND gate
- 7411 triple 3-input AND gate
- 7432 quad 2-input OR gate

## 1.2 Part 2

For the pure logic gate implementations, we will assume a 22 nanosecond delay for each AND, OR, and NOT gate. The propagation delays for the 74xx series ICs are as follows:

- 7404: 22 ns
- 7408: 22 ns
- 7411: 22 ns
- 7432: 22 ns

Thus, the propagation delays for the implementations of  $F$  and  $G$  are as follows:

- $F$  (logic gates): 22 ns + 22 ns = 44 ns
- $G$  (logic gates): 22 ns + 22 ns + 22 ns = 66 ns
- $F$  (74xx series ICs): 22 ns + 22 ns = 44 ns
- $G$  (74xx series ICs): 22 ns + 22 ns + 22 ns = 66 ns

## 1.3 Part 3

Switching characteristics of 7404 hex inverter at  $V_{cc} = 5V$  and  $25^\circ C$ :

Symbol	Parameter	Conditions	Min	Typ	Max	Units
t <sub>plh</sub>	Propagation Delay Time LOW-to-HIGH Level Output	Cl=15pF Rl=400R			22	ns
t <sub>phl</sub>	Propagation Delay Time HIGH-to-LOW Level Output	Cl=15pF Rl=400R			15	ns

Switching characteristics of 7408 quad 2-input AND gate at  $V_{cc} = 5V$  and  $25^\circ C$ :

Symbol	Parameter	Conditions	Min	Typ	Max	Units
t <sub>plh</sub>	Propagation Delay Time LOW-to-HIGH Level Output	Cl=15pF Rl=400R			22	ns
t <sub>phl</sub>	Propagation Delay Time HIGH-to-LOW Level Output	Cl=15pF Rl=400R			15	ns

Switching characteristics of 7411 triple 3-input AND gate at  $V_{cc} = 5V$  and  $25^\circ C$ :

Symbol	Parameter	Conditions	Min	Typ	Max	Units
t <sub>plh</sub>	Propagation Delay Time LOW-to-HIGH Level Output	Cl=15pF Rl=400R			22	ns
t <sub>phl</sub>	Propagation Delay Time HIGH-to-LOW Level Output	Cl=15pF Rl=400R			15	ns

Switching characteristics of 7432 quad 2-input OR gate at  $V_{cc} = 5V$  and  $25^\circ C$ :

Symbol	Parameter	Conditions	Min	Typ	Max	Units
t <sub>plh</sub>	Propagation Delay Time LOW-to-HIGH Level Output	Cl=15pF Rl=400R			22	ns
t <sub>phl</sub>	Propagation Delay Time HIGH-to-LOW Level Output	Cl=15pF Rl=400R			15	ns

## 2 Problem 2

### 2.1 Part 1

1. The number of input bits is 10 since there are 10 cars with switches.
2. We will need 7 output bits for the 7-segment display. We do not need to use the 8th decimal point input, since we have 10 cars represented from 0 to 9.
3. We will need a 4-bit data bus between the encoder and decoder, since  $\lceil \log_2 10 \rceil = 4$ .